

Exercises

- 6.8 The voltage across a $12\text{-}\mu\text{F}$ capacitor is shown in Fig. P6.8. Compute the waveform for the current in the capacitor.

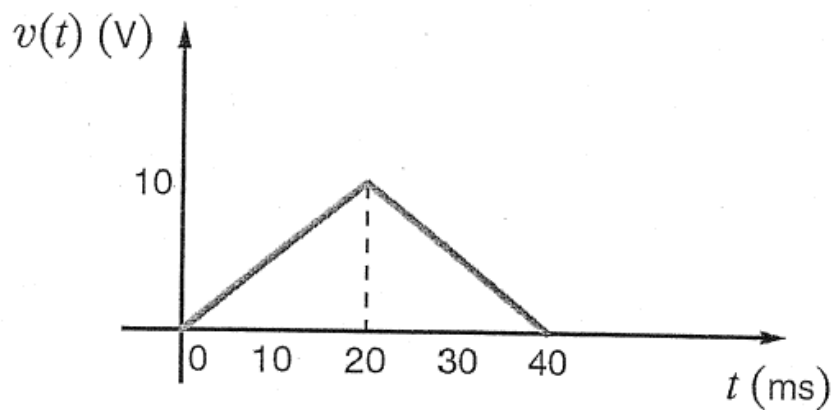


Figure P6.8

- 6.10 The voltage across a $50\text{-}\mu\text{F}$ capacitor is shown in Fig. P6.10. Compute the waveform for the current in the capacitor.

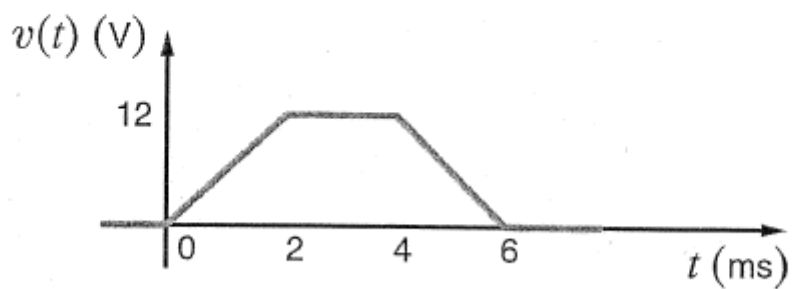


Figure P6.10

- 6.17 The waveform for the current in a $50\text{-}\mu\text{F}$ capacitor is shown in Fig. P6.17. Determine the waveform for the capacitor voltage. **PSV**

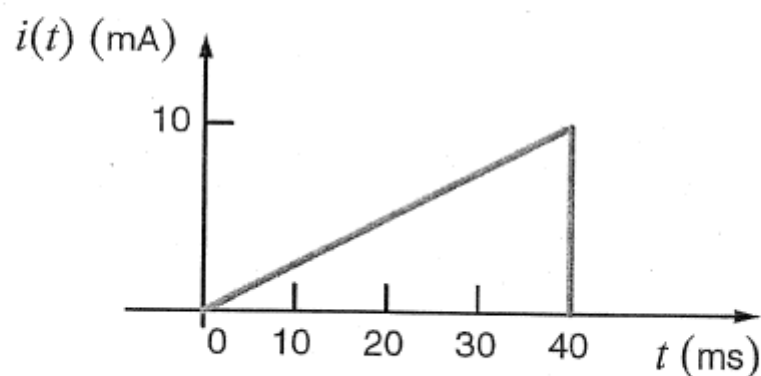


Figure P6.17

- 6.28 The current in a 50-mH inductor is shown in Fig. P6.28. Find the voltage across the inductor. **PSV**

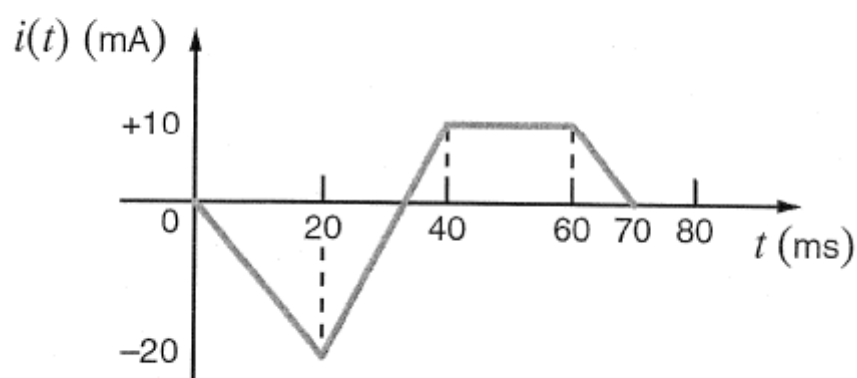


Figure P6.28

- 6.51 Select the value of C to produce the desired total capacitance of $C_T = 1\ \mu\text{F}$ in the circuit in Fig. P6.51.

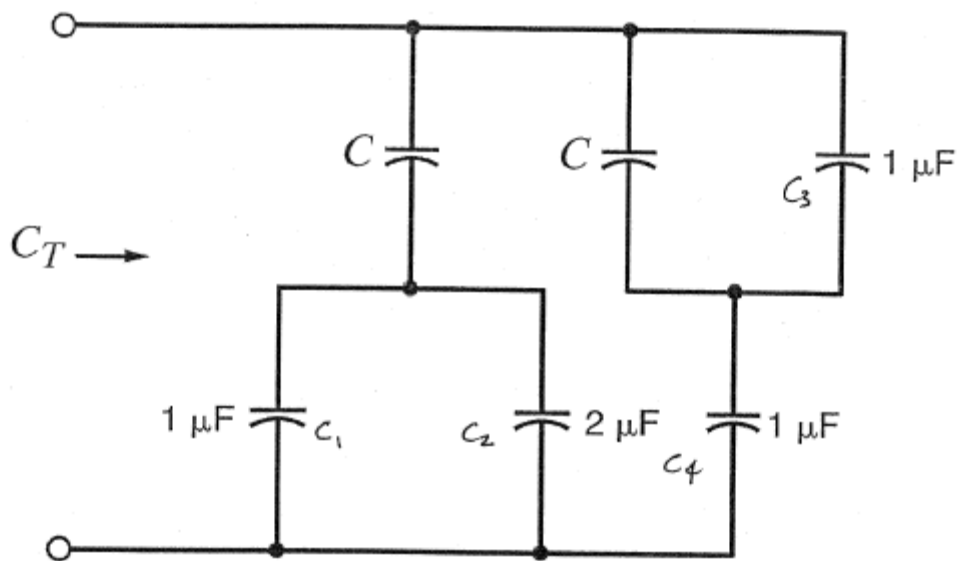


Figure P6.51

- 6.52 Find C_T in the network in Fig. P6.52 if (a) the switch is open and (b) the switch is closed.

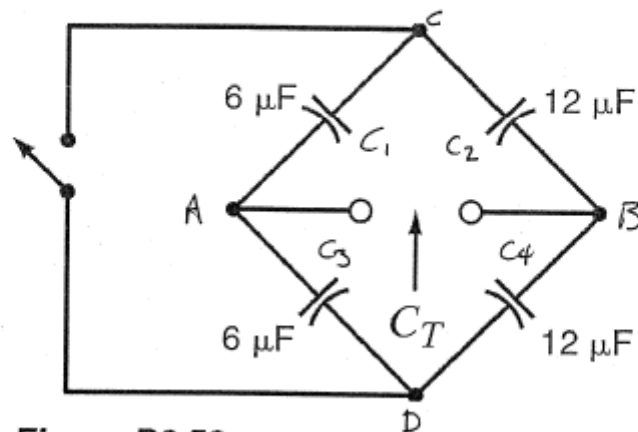


Figure P6.52

- 6.66** Determine the inductance at terminals A - B in the network in Fig. P6.66. **PSV**

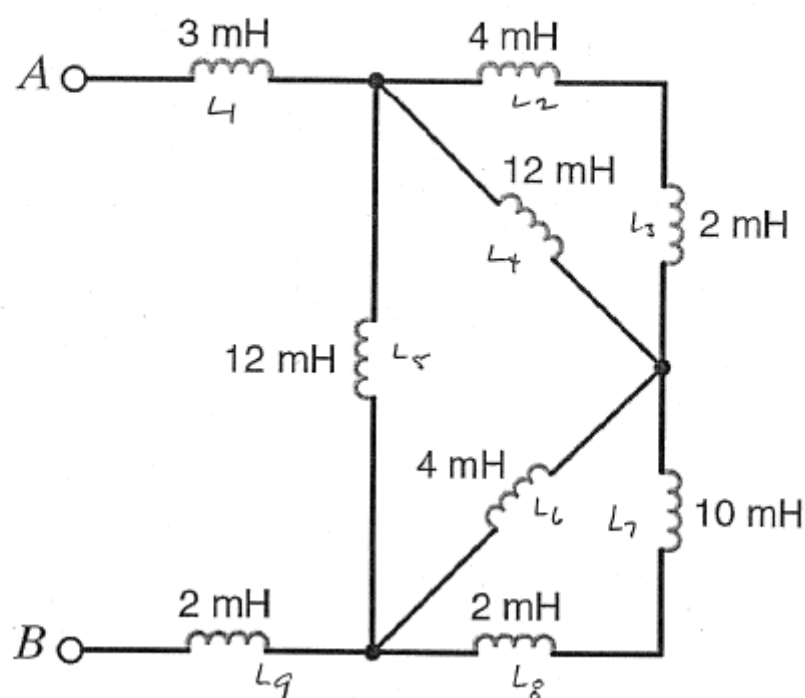


Figure P6.66

- 6.67** Determine the inductance at terminals A - B in the network in Fig P6.67. **CS**

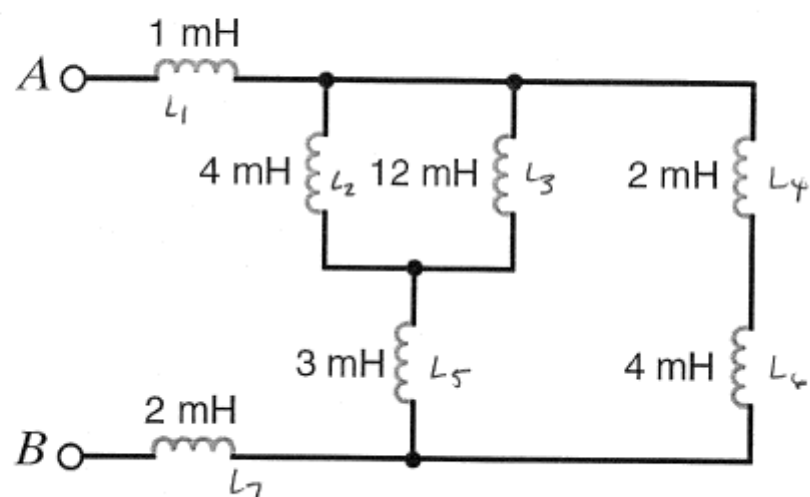


Figure P6.67

- 7.6** Use the differential equation approach to find $v_o(t)$ for $t > 0$ in the circuit in Fig. P7.6 and plot the response including the time interval just prior to opening the switch. **CS**



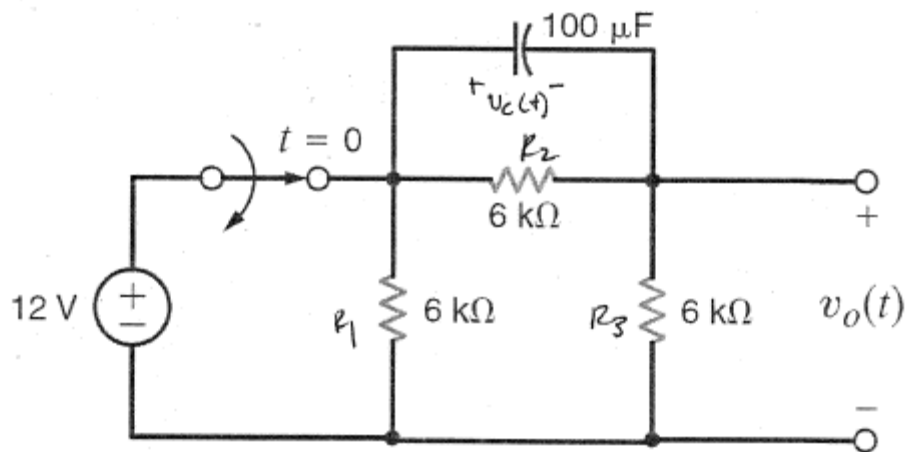


Figure P7.6

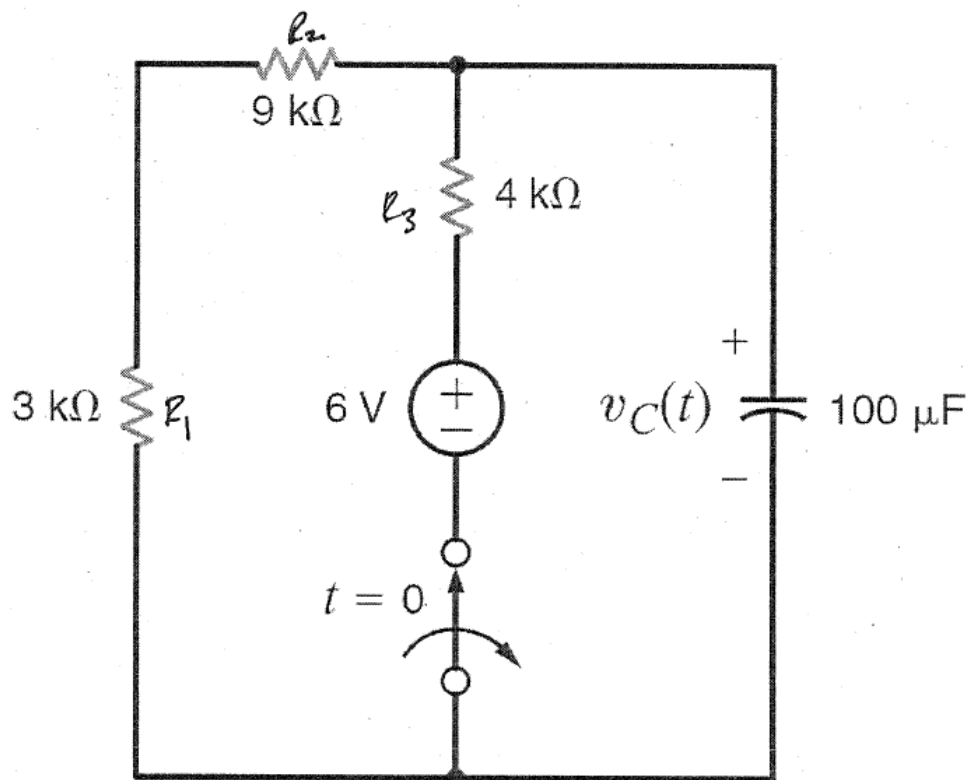Use the differential equation approach to find $v_C(t)$ for $t > 0$ in the circuit in Fig. P7.4.



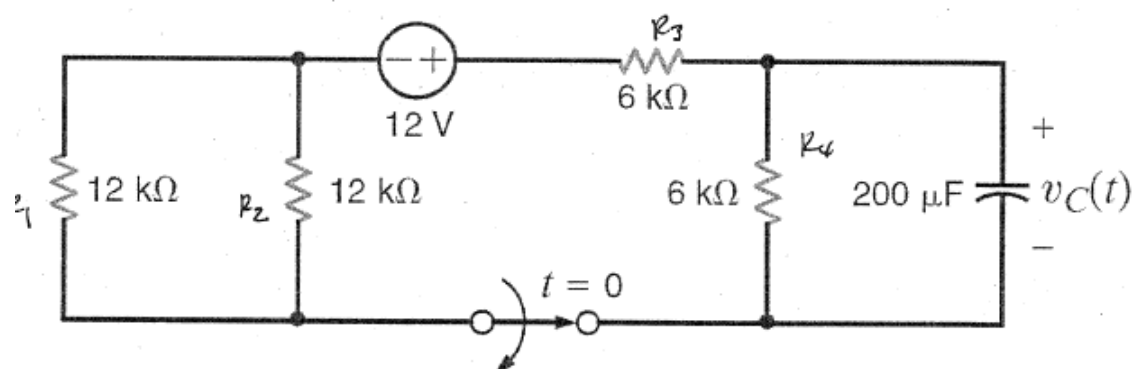7.5 Use the differential equation approach to find $v_C(t)$ for $t > 0$ in the circuit in Fig. P7.5 and plot the response including the time interval just prior to opening the switch. **CS**



7.4 Use the differential equation approach to find $v_C(t)$ for $t > 0$ in the circuit in Fig. P7.4.

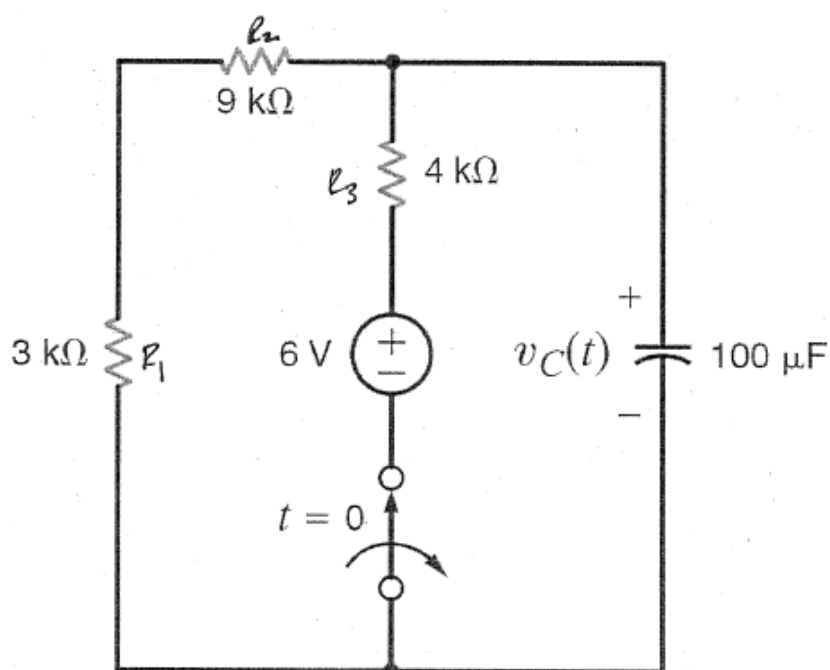


Figure P7.4

- 7.5** Use the differential equation approach to find $v_C(t)$ for $t > 0$ in the circuit in Fig. P7.5 and plot the response including the time interval just prior to opening the switch. **CS**

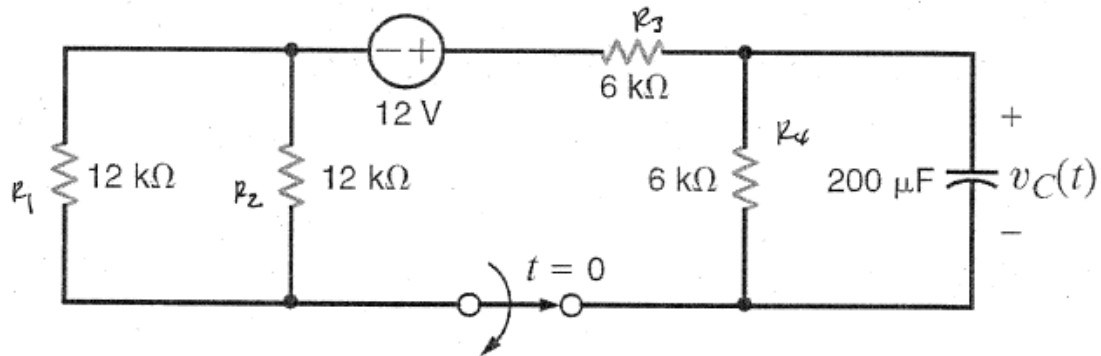


Figure P7.5

- 7.80** For the underdamped circuit shown in Fig. P7.80, determine the voltage $v(t)$ if the initial conditions on the storage elements are $i_L(0) = 1$ A and $v_C(0) = 10$ V. **CS**

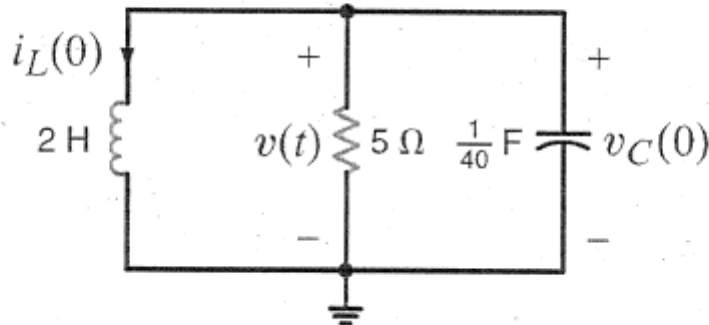


Figure P7.80

- 7.84 Find $v_C(t)$ for $t > 0$ in the circuit in Fig. P7.84 if $v_C(0) = 0$.

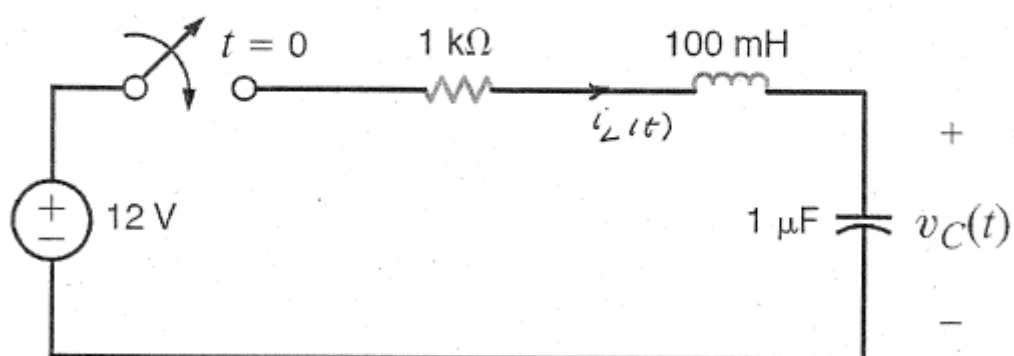


Figure P7.84